

**CS223: Digital Design**

**Section 01**


**Lab 4**

**Efe Beydoğan**

**21901548**

**28.11.2020**

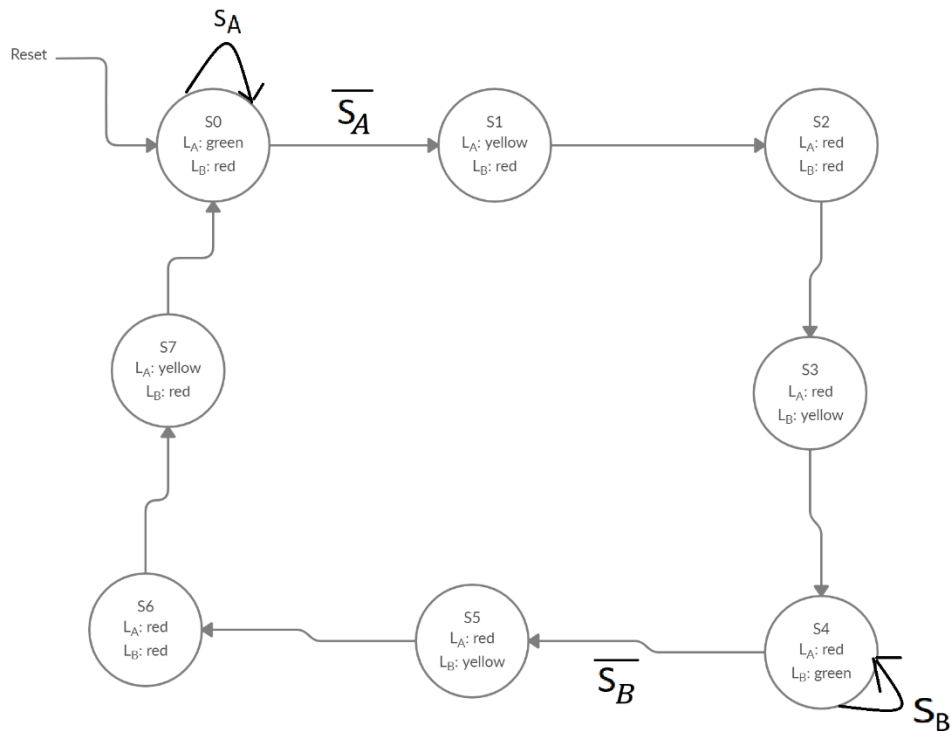**a) Sketch your improved Moore state machine transition diagram, state encodings, state transition table, output table, next state and output equations and your Finite State Machine schematic:**



| state | encoding<br>$s_{1:0}$ |
|-------|-----------------------|
| S0    | 000                   |
| S1    | 001                   |
| S2    | 010                   |
| S3    | 011                   |
| S4    | 100                   |
| S5    | 101                   |
| S6    | 110                   |
| S7    | 111                   |

| current state |       |       | inputs |       | next state |        |        |
|---------------|-------|-------|--------|-------|------------|--------|--------|
| $s_2$         | $s_1$ | $s_0$ | $s_a$  | $s_b$ | $s'_2$     | $s'_1$ | $s'_0$ |
| 0             | 0     | 0     | 0      | X     | 0          | 0      | 1      |
| 0             | 0     | 0     | 1      | X     | 0          | 0      | 0      |
| 0             | 0     | 1     | X      | X     | 0          | 1      | 0      |
| 0             | 1     | 0     | X      | X     | 0          | 1      | 1      |
| 0             | 1     | 1     | X      | X     | 1          | 0      | 0      |
| 1             | 0     | 0     | X      | 1     | 1          | 0      | 0      |
| 1             | 0     | 0     | X      | 0     | 1          | 0      | 1      |
| 1             | 0     | 1     | X      | X     | 1          | 1      | 0      |
| 1             | 1     | 0     | X      | X     | 1          | 1      | 1      |
| 1             | 1     | 1     | X      | X     | 0          | 0      | 0      |

| Output | Encoding $L_{2:0}$ |
|--------|--------------------|
| Green  | 011                |
| Yellow | 001                |
| Red    | 111                |

| current state |       |       | outputs  |          |          |          |          |          |
|---------------|-------|-------|----------|----------|----------|----------|----------|----------|
| $s_2$         | $s_1$ | $s_0$ | $L_{a2}$ | $L_{a1}$ | $L_{a0}$ | $L_{b2}$ | $L_{b1}$ | $L_{b0}$ |
| 0             | 0     | 0     | 0        | 1        | 1        | 1        | 1        | 1        |
| 0             | 0     | 1     | 0        | 0        | 1        | 1        | 1        | 1        |
| 0             | 1     | 0     | 1        | 1        | 1        | 1        | 1        | 1        |
| 0             | 1     | 1     | 1        | 1        | 1        | 0        | 0        | 1        |
| 1             | 0     | 0     | 1        | 1        | 1        | 0        | 1        | 1        |
| 1             | 0     | 1     | 1        | 1        | 1        | 0        | 0        | 1        |
| 1             | 1     | 0     | 1        | 1        | 1        | 1        | 1        | 1        |
| 1             | 1     | 1     | 0        | 0        | 1        | 1        | 1        | 1        |

### Output Equations:

$$L_{a2} = (S_1 \oplus S_2) + S_1 \bar{S}_0$$

$$L_{a1} = (S_1 \oplus S_2) + \bar{S}_0$$

$$L_{a0} = 1$$

$$L_{b2} = (\bar{S}_2 \oplus \bar{S}_1) + \bar{S}_2 \bar{S}_0$$

$$L_{b1} = (\bar{S}_2 \oplus \bar{S}_1) + \bar{S}_0$$


$$L_{b0} = 1$$

### Next State Equations:

$$S_2' = S_2(\bar{S}_1 + \bar{S}_0) + \bar{S}_2 S_1 S_0$$

$$S_1' = S_1 \oplus S_0$$
 
$$S_0' = \bar{S}_0 (S_1 + \bar{S}_2 \bar{S}_A + S_2 \bar{S}_B)$$



**b) How many flip-flops are needed to implement this problem?**

Since there are 3 state bits, 3 flip-flops are needed to implement this problem.

**c) How many rising edges do you need to count from the Basys3 clock in order to obtain such frequency? Write the SystemVerilog code that will count original clock cycles output HIGH in every 3 seconds.**

The clock changes state  $10^8$  times in a second, so it changes state  $3 \times 10^8$  times in 3 seconds. Half of those state changes are rising edges where the clock goes from 0 to 1. So, we need to count  $\frac{3 \times 10^8}{2} = 15 \times 10^7$  rising edges from the BASYS3 clock to obtain a 3 second delay.

**SystemVerilog code for the clock:**

```
module clock_counter( input clk, input reset, output logic clock);
```

```
localparam number = 150000000;
```

```
logic [31:0] count;
```

```
always @ (posedge(clk), posedge(reset))
```

```
begin
```

```
if (reset == 1'b1)
```

```
count <= 32'b0;
```

```
else if (count == number - 1)
```

```
count <= 32'b0;
```

```
else
```

```
count <= count + 1;
```

```
end
```

```
always @ (posedge(clk), posedge(reset))
```

```
begin
```

```
if (reset == 1'b1)
```

```
clock <= 1'b0;
```

```
else if (count == number - 1)
```

```
clock <= ~clock;
```

```
else
```

```
clock <= clock;
```

```
end
```

```
endmodule
```

**d) Write the SystemVerilog code for your traffic light system and a testbench for it:**

**SystemVerilog code for the traffic light system:**

```
module traffic_light_system( input logic clk, input logic reset, input logic Sa, Sb, output logic [2:0] La, Lb);
```

```
    typedef enum logic [2:0] {S0, S1, S2, S3, S4, S5, S6, S7} statetype;
```

```
    statetype state, nextstate;
```

```
    // state register
```

```
    always_ff @(posedge clk, posedge reset)
```

```
    if (reset) state <= S0;
```

```
    else state <= nextstate;
```

```
    // next state logic
```

```
    always_comb
```

```
    case (state)
```

```
        S0: if (Sa) nextstate = S0;
```

```
            else nextstate = S1;
```

```
        S1: nextstate = S2;
```

```
        S2: nextstate = S3;
```

```
        S3: nextstate = S4;
```

```
        S4: if (Sb) nextstate = S4;
```

```
            else nextstate = S5;
```

```
        S5: nextstate = S6;
```

```
        S6: nextstate = S7;
```

```
        S7: nextstate = S0;
```

```
        default: nextstate = S0;
```

```
    endcase
```

```

// output logic

logic n0, n1;

xor( n0, state[1], state[2]);

assign La[2] = n0 | (state[1] & ~state[0]);
assign La[1] = n0 | ~state[0];
assign La[0] = 1;

assign Lb[2] = ~n0 | (~state[2] & ~state[0]);
assign Lb[1] = ~n0 | ~state[0];
assign Lb[0] = 1;

endmodule

Testbench:

module testbench_traffic();

    logic clk, reset, Sa, Sb;

    logic [2:0] La, Lb;

    // instantiate device under test

    traffic_light_system dut(clk, reset, Sa, Sb, La, Lb);

    // apply inputs one at a time

    always
    begin
        clk = 1; #10;

        clk = 0; #10;

    end

```

```

initial begin

    reset = 1; Sa = 1; Sb = 0; #10;

    reset = 0; #100;

    Sb = 1; #100;

    Sa = 0; #100;

    Sa = 0; Sb = 0; #100;

end

endmodule

```

**e) Write the SystemVerilog code for the top design where you will combine the new clock generator in part c and traffic light system in part d:**

```

module clock_fsm(input logic clk, reset, Sa, Sb, output logic [2:0] La, Lb);

    logic clock;

    clock_counter clockdiv(clk, reset, clock);

    traffic_light_system fsm(clock, reset, Sa, Sb, La, Lb);

endmodule

```