 


CS223 – DIGITAL DESIGN



HOMEWORK # 2

Q1. Given the logic function $F(w, x, y, z) = \sum m(0, 1, 2, 6, 10, 13) + \sum d(4, 8, 15)$ where m represents minterms of the function and d represents don't cares. Find the minimal (optimal) Boolean expression for F using the Karnaugh map method.


Q2. Find a minimal Boolean expression for the function given in the following Karnaugh map. Implement the function F using only NOR gates assuming that the complements of input variables are available.



  
Q3. Design a 4-bit left shifter using only eight 2:1 multiplexers. The shifter accepts a 4-bit input $A_{3:0}$ and a 2-bit shift amount $S_{1:0}$. It produces a 4-bit output $Y_{3:0}$. Write the truth table and sketch the circuit schematic using the multiplexer symbol given below.



 
Q4. You will design an 8-bit synchronous Up/Down counter. The inputs are CLK, Reset, and Up. When Reset is 1, the output bits $C_{7:0}$ are all 0. Otherwise, when **Up** = 1, the circuit **counts up**, and when **Up** = 0, the circuit **counts down**. You can use only one 8-bit **register** with reset input, one 8-bit **adder**, and one 8-bit 2:1 **multiplexer**. Sketch the circuit schematic of your design using the component symbols given below.




Register

 

Adder

 

Multiplexer

 

$$F = \bar{B}C + CD + A\bar{D} + \bar{A}B\bar{C}$$


$$F = (A + \bar{B} + \bar{C} + D)(A + B + C)(\bar{A} + C + \bar{D})$$

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Q5. For the logic function $F = BD(\bar{A} + C) + A(C + \bar{D}) + (B + \bar{C})(A + \bar{B} + C + D)$

(a) Write the truth table.

 (b) Write the function in Sum-of-Products (SOP) and Product-of-Sums (POS) canonical forms.



binary numbers as the number of bit positions that the
 mple.

x_2	x_1	x_0	z_1	z_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


 between 001 and 100 is 2 since they
 s 3 since they differ in three-bit
 000 differ in one-bit position.

take numbers ($A_2A_1A_0$ and $B_2B_1B_0$)
 y nu output. The output will give the
 . For example, if the inputs are $A_2A_1A_0 = 101$ and

$B_2B_1B_0 = 011$, then the output will be $Z_2Z_1Z_0 = 10$ indicating that the distance is equal to 2.


Draw the logic diagram of your circuit. You can use **only** AND, OR, NOT, and XOR gates.

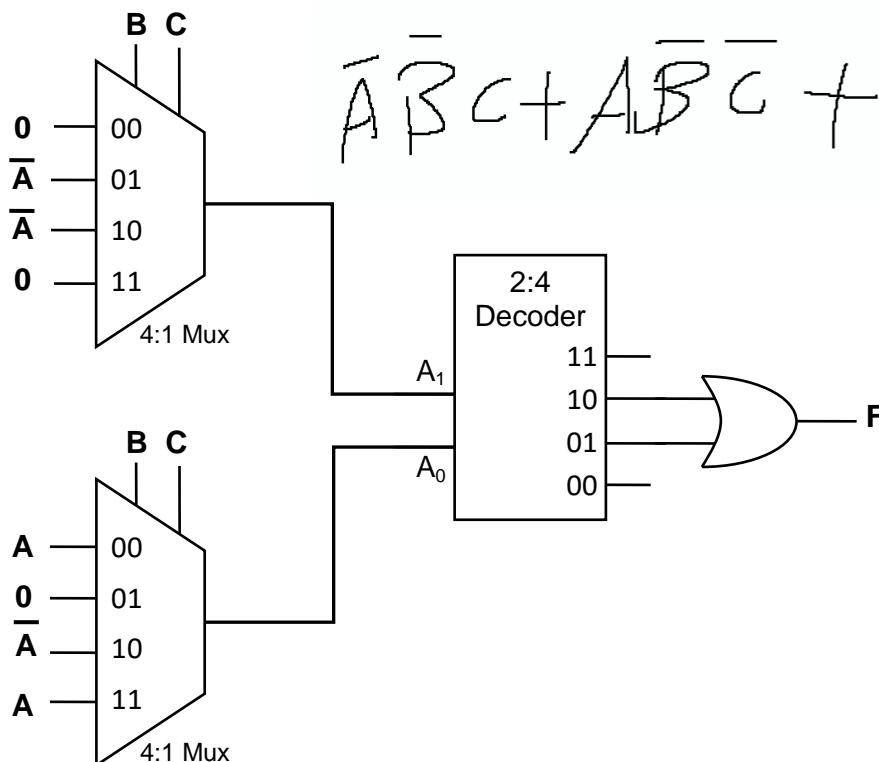Q7. Find the minimized Boolean expression for the logic function performed by the following circuit (inputs are A, B, C and the output is F).



$$\bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C$$

 Q8. Design a circuit that will take two 8-bit numbers A and B and produce their two's complement. Use two's complement form. Show your design clearly by drawing the logic gates.



presented by using 8-bit numbers in logic gates. Show your design.

Q9. The state transition diagram of an FSM is given below. The FSM receives two inputs A , B and it has one output Y .


(a) Write the state transition and output table using binary state encodings.

(b) Write the minimized Boolean equations for the next-state logic and output logic.

$$S_1' = \bar{S}_1 S_0 B + S_1 \bar{S}_0 A$$

$$S_0' = \bar{S}_1 \bar{S}_0 A$$

$$Y = S_1 A$$

 


S_1	S_0	A	B	S_1'	S_0'	Y
0	0	0	X	0	0	0
0	0	1	X	0	1	0
0	1	X	0	0	0	0
0	1	X	1	1	0	0
1	0	0	X	0	0	0
1	0	1	X	1	0	1

Q10. Analyze the Finite State Machine (FSM) given below.

(a) Write the state table and output table for the FSM using binary state encodings.

 (b) Sketch the state transition diagram of the FSM.




$$S_1' = S_0 \oplus (A \oplus B)$$

$$S_0' = S_0 (A \oplus B) + \bar{A} B$$


$$Y = S_1$$

S_1	S_0	Y
0	0	0
0	1	0
1	0	1
1	1	1

S_1	S_0	A	B	S_1'	S_0'	Y
0	0	0	0	0	0	0
0	0	0	1	0	1	0
0	0	1	0	1	0	0
0	0	1	1	1	1	0
0	1	0	0	0	0	0
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	1	0
1	0	0	0	0	0	0
1	0	0	1	0	1	0
1	0	1	0	1	0	1
1	0	1	1	1	1	1
1	1	0	0	0	0	0
1	1	0	1	0	1	0
1	1	1	0	1	0	1
1	1	1	1	1	1	1



 


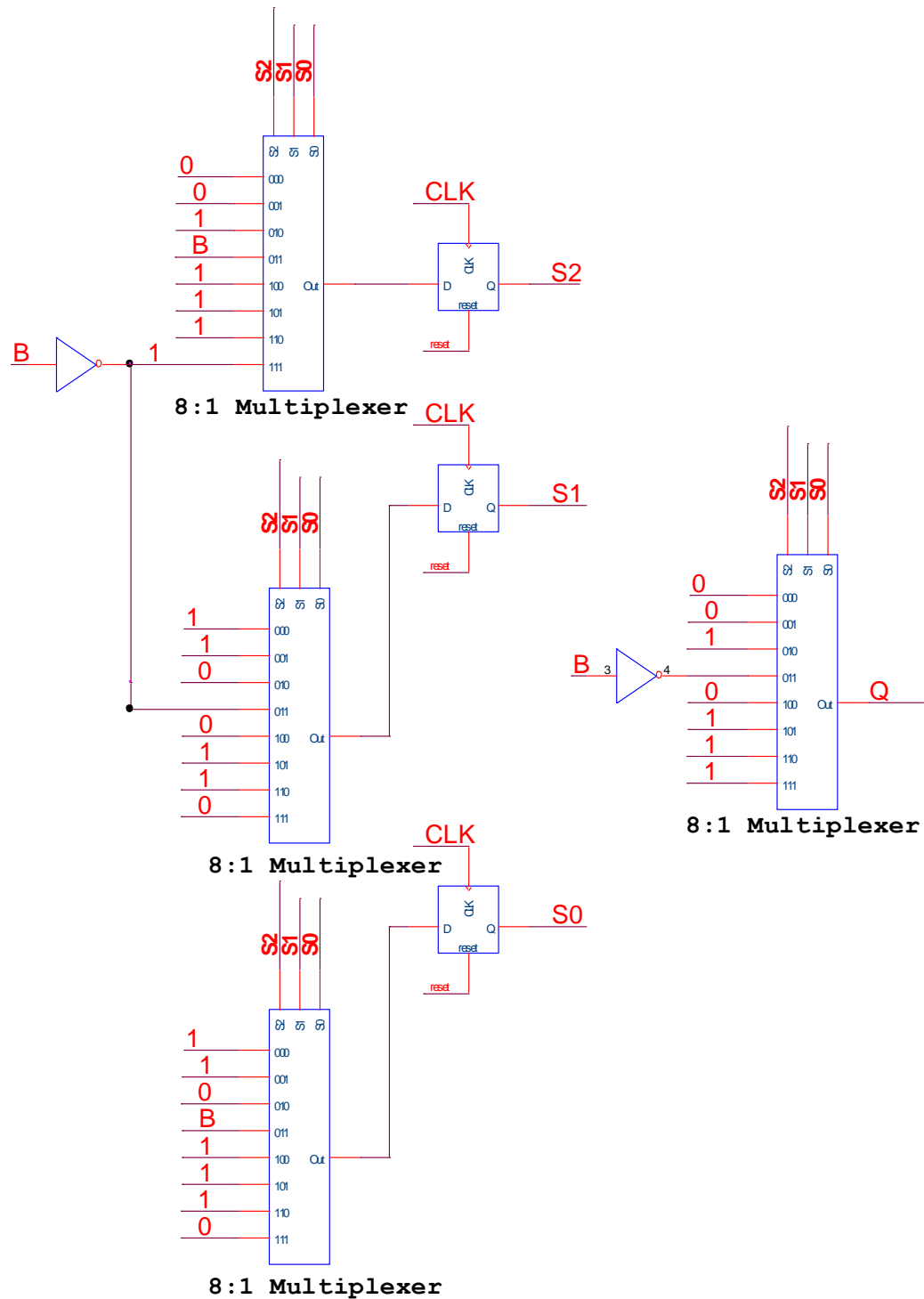Q11. For the sequential circuit (FSM) given below (**B** is the input, **Q** is the output)



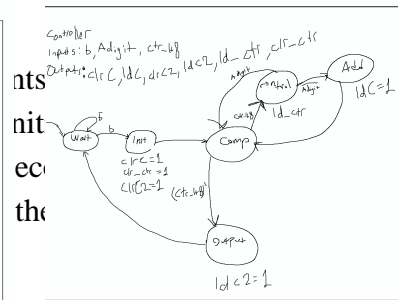  
(a) Write the Boolean equations for the next-state and output logic in sum-of-products form.

$$\begin{aligned}
 S'_2 &= \bar{S}_1 \bar{S}_0 + S_1 \bar{S}_0 + S_2 \bar{S}_1 + S_2 \bar{B} + \bar{S}_2 S_0 B \\
 S'_1 &= \bar{S}_2 \bar{S}_1 + \bar{S}_1 \bar{S}_0 + \bar{S}_2 S_1 \bar{B} + S_2 S_1 \bar{S}_0 \\
 S'_0 &= \bar{S}_1 + S_2 \bar{S}_0 + \bar{S}_2 S_1 B \\
 Q &= S_1 \bar{S}_0 + S_1 \bar{B} + S_2 S_0
 \end{aligned}$$





it input A
ts when a
nd then it
b changes


 
- (b) Create a datapath for your HLSM. Label the input
- (c) Connect the datapath to the controller and show a
- (d) Derive the FSM and draw the state transition diag



  Q15. For the HLSM given below, complete the RTL design process. Create a datapath with each component clearly labeled and show the connections between the datapath to the controller and show all signals between the datapath and the controller.



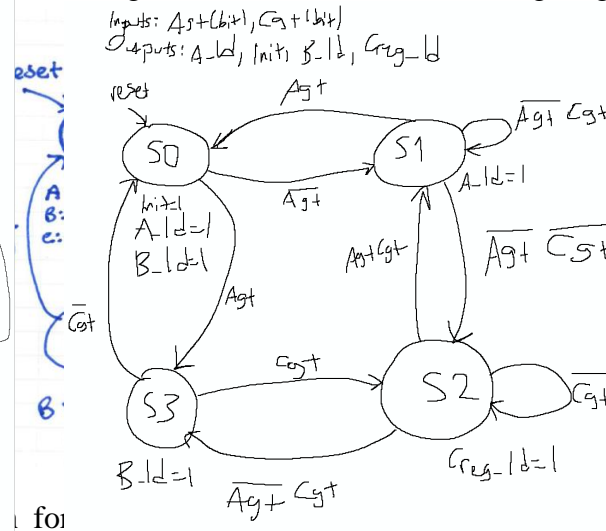 Q16. The state transition diagram for an HLSM is given below. The output C (32 bit) comes from a register of the same name (Creg). A and B are 8-bit local storage registers.




its and outputs of the

datapath. For each component in the datapath, clearly identify it to show its function, name its inputs and

S1	S0	Agt	Cgt	S'1	S'0
0	0	0	x	0	1
0	0	1	x	1	1
0	1	0	0	1	0
0	1	0	1	0	1
0	1	1	x	0	0
1	0	0	1	1	1
1	0	x	0	1	0
1	0	1	1	0	1
1	1	x	0	0	0
1	1	x	1	1	0

(b) Derive the FSM and draw the state transition diagram. Write the state transition and output tables using binary state encodings (Hint: You can use a shorthand notation Agt for $A > B$ and Cgt for $C > A+B$).

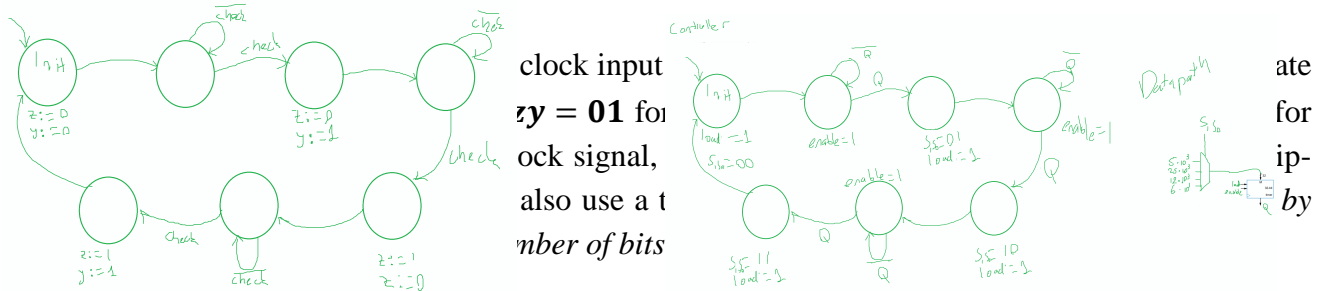(c) Write the minimized Boolean equations for the next state and output of FSM.



Q18. The state transition diagram of an FSM is given below. You will design the controller for this FSM using only two 4:1 multiplexers and two 2:1 multiplexers.

S_1	S_0	X	S_1'	S_0'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	0

S_1	S_0	Z_1	Z_0
0	0	1	0
0	1	1	0
1	0	0	1
1	1	0	0

Handwritten equations for Q18:


$$S_1' = X$$

$$S_0' = \bar{S}_0 S_1 + \bar{S}_0 X + S_1 S_0 X$$

$$Z_1 = \bar{S}_1$$

$$Z_0 = S_1 \bar{S}_0$$

 Additional notes: $Z_1 Z_0 = 10$, $Z_1 Z_0 = 01$, $X=1$, $Z_1 Z_0 = 00$.




- Write the state transition table and output table for the FSM using binary state encodings.
- Write the Boolean equations for the next state and output of FSM.
- Sketch the circuit schematic of FSM using state register, two 4:1 multiplexers, and two 2:1 multiplexers. Don't use any logic gate. You can use the logic levels 1 and 0 as input.

Q19. Design a Finite State Machine (FSM) using the state transition diagram given below

S_1	S_0	A	B	S_1'	S_0'
0	0	0	X	0	0
0	0	1	X	0	1
0	1	X	0	0	0
0	1	X	1	1	0
1	0	X	X	0	0

S_1	S_0	Q
0	0	0
0	1	0
1	0	1

 - Using binary $S_1' = \bar{S}_1 S_0 B$ $Q = S_1$
Write Boolean $S_0' = \bar{S}_1 \bar{S}_0 A$
- Sketch a schematic for the FSM.



Q20. A register file has 16 registers each having 16 bits. The registers RF[0] to RF[15] contain positive or negative integers. Design an HLSM which will find the sum of absolute values of the 16 integers stored in RF[0] to RF[15]. The negative numbers are in 2's complement form. The sum is going to be stored in a separate **SUM** register. Upon reset, the HLSM will be in the initial state waiting for the **GO** signal. When the operation is completed the HLSM will return to its initial state and wait for a GO signal to start over again. *Show your design clearly.*

- Capture the system behavior as an HLSM and draw the state transition diagram.
- Design the datapath for this HLSM. Specify each component in the datapath clearly (i.e. name of the component, input signals, output signals, number of bits, etc.).
- Connect the datapath to the controller (FSM) and show the signals between the controller and the datapath.
- Derive the FSM and draw the state transition diagram.

