

CS223: Digital Design

Section 01

Lab 5

Efe Beydoğan

21901548

12.12.2020



a) Show the ReduceSum HLSM. Show also the controller/datapath diagram for it:



ReduceSum HLSM:

Inputs: enable (bit), number (8 bit)

Outputs: Sum (12 bit), read Address (4 bit)

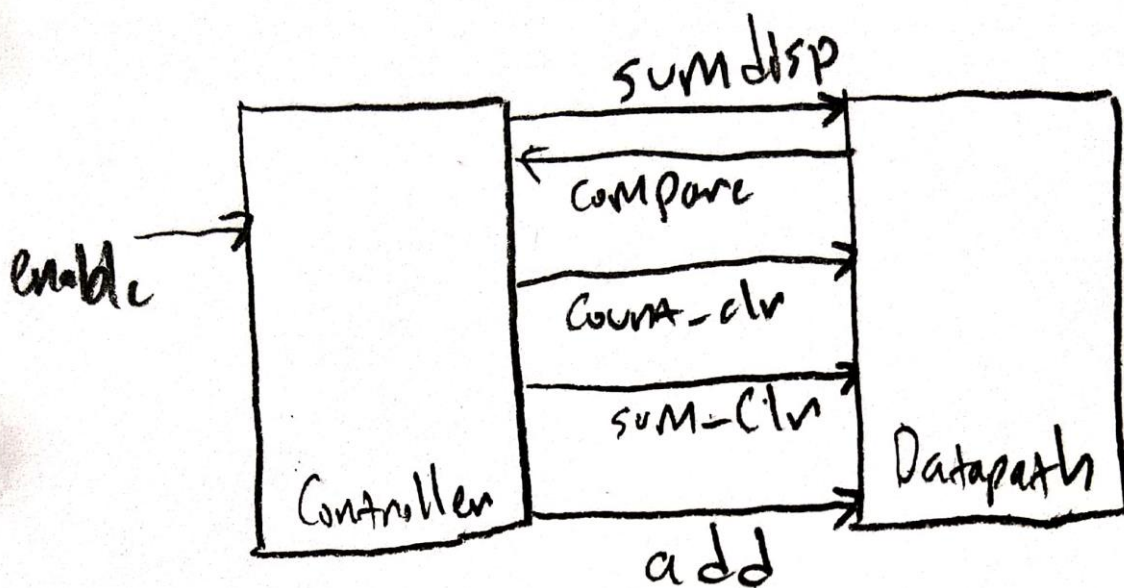 Local storage: count (5 bit), Sum (12 bit), constant (5 bit)



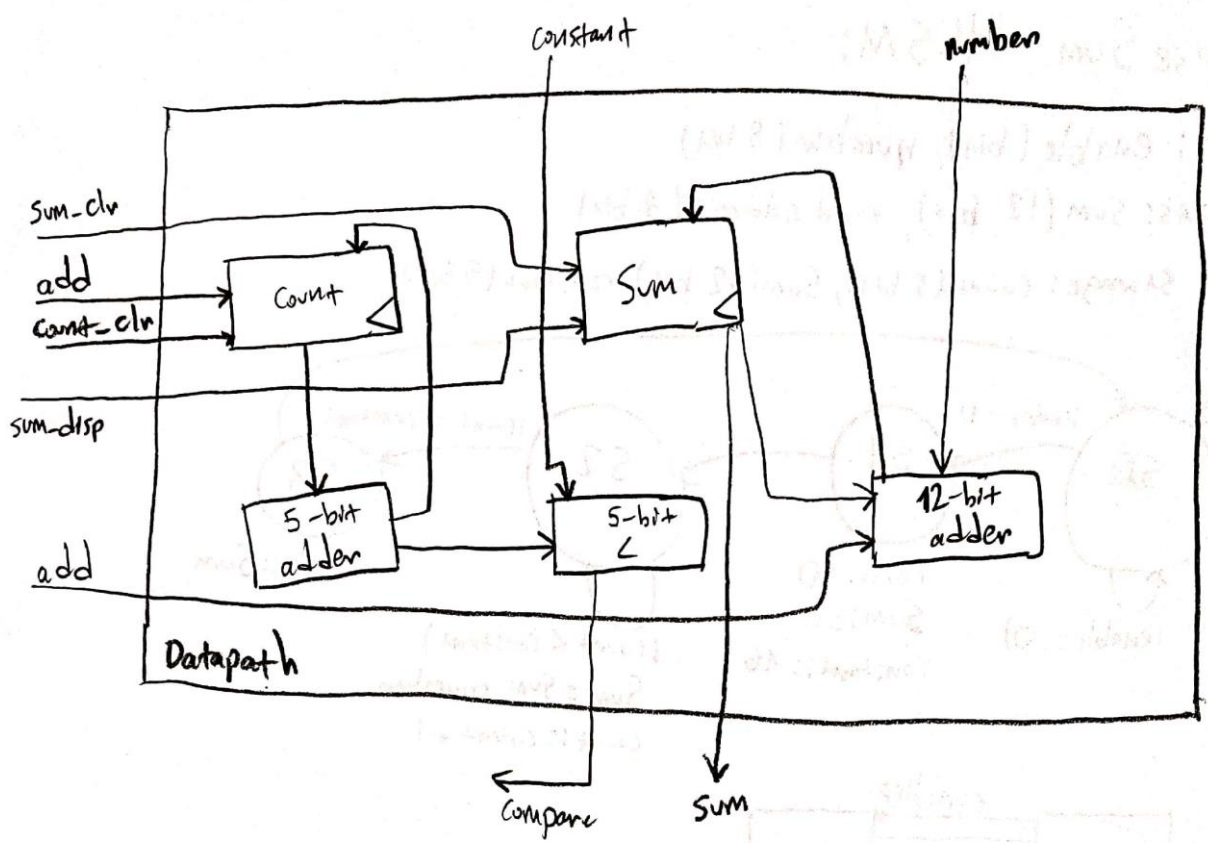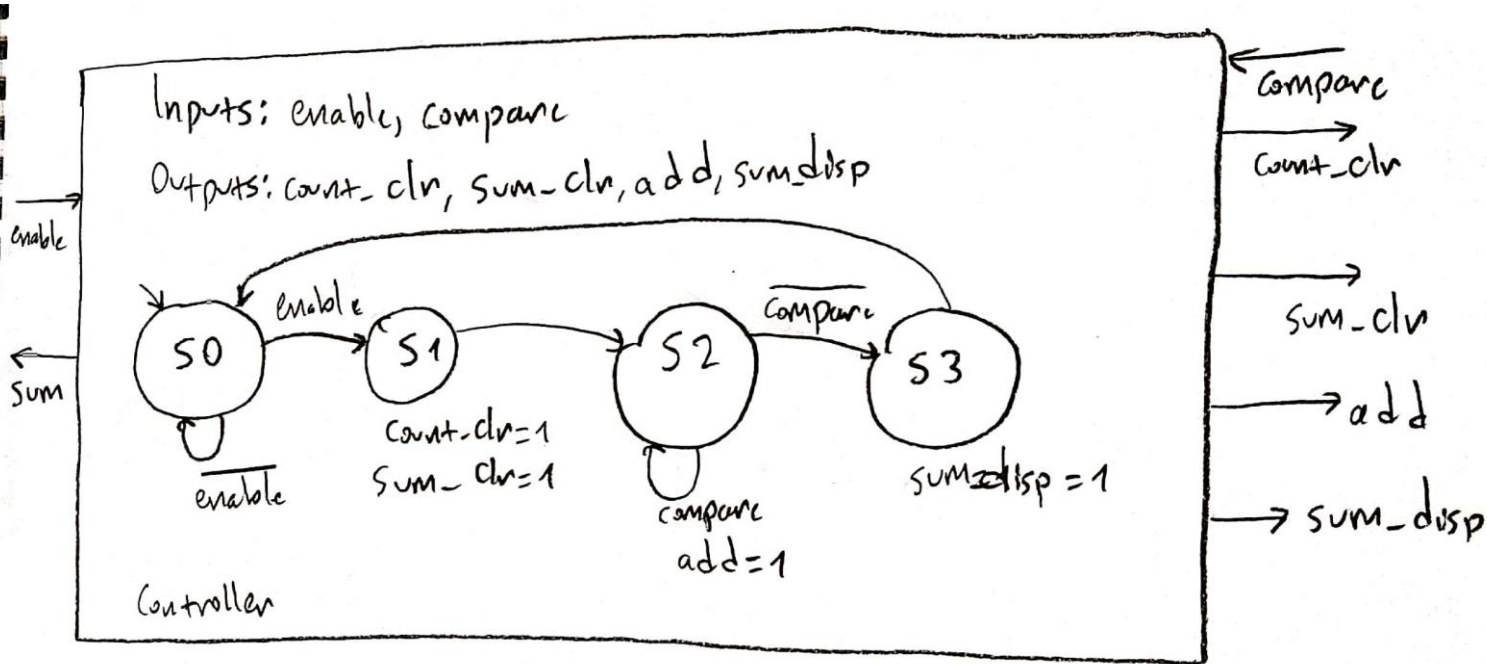

b) You will be given a debouncer module for your pushbuttons. Research and explain briefly why there is a need for such a circuit:

A button normally outputs 1 when pressed, and outputs 0 when not pressed. However, since the button is a mechanical device, pressing it down may cause a small amount of bounce as the button settles in the down position. When it is first pressed, before outputting 1 constantly, the button first goes back and forth between 1 and 0 outputs. In order to prevent this, a debouncer is needed to preserve the output as 1 for an amount of time which is enough for the button to settle in its down position. This settling down usually takes about a few milliseconds, so the debouncer should hold the output of 1 for a small amount of time before the button settles.

c) Write the SystemVerilog Code for your memory module. Write a testbench for it:

Code for memory module:

```
`timescale 1ns / 1ps
```

```
module memory_module(input logic clk, writeEnable, input logic [3:0] writeAddress, input logic [7:0]
writeData, input logic [3:0] readAddress1, input logic [3:0] readAddress2, output logic [7:0]
readData1, output logic [7:0] readData2);
```

```
    logic [7:0] RAM[15:0]; // 16x8 memory module
```

```
    always_ff @(posedge clk)
```

```
    begin
```

```
        if ( writeEnable)
```

```
            RAM[writeAddress] <= writeData;
```

```
    end
```

```
    assign readData1 = RAM[readAddress1];
```

```
    assign readData2 = RAM[readAddress2];
```

```
endmodule
```

Testbench for memory module:

```
`timescale 1ns / 1ps
```

```
module memorymodule_testbench();
```

```
    logic clk, writeEnable;
```

```
    logic [3:0] writeAddress;
```

```
    logic [7:0] writeData;
```

```
    logic [3:0] readAddress1;
```

```
    logic [3:0] readAddress2;
```

```
    logic [7:0] readData1;
```

```
    logic [7:0] readData2;
```

```
    memory_module dut( clk, writeEnable, writeAddress, writeData, readAddress1, readAddress2,  
readData1, readData2);
```

```
    always
```

```
    begin
```

```
        clk = 1; #1;
```

```
        clk = 0; #1;
```

```
    end
```

```
    initial begin
```

```
        // writeEnable = 0; #5;
```

```
        writeEnable = 1;
```

```
        writeAddress = 4'b0;
```

```
        writeData = 8'b0;
```

```
        readAddress1 = 4'b0;
```

```
        readAddress2 = 4'b0;
```

```
        for ( int i = 4'b0; i < 5'b10000; i++) begin
```

```

        #10;

        writeAddress = i;

        if ( i != 4'b0)

            writeData = writeData + 1;


        readAddress1 = i;

        readAddress2 = i;

        #10;

    end

end

endmodule

```

d) Write the SystemVerilog Code for your ReduceSum Module. Write a testbench for it:

Code for ReduceSum module:

```

`timescale 1ns / 1ps

```

```

module ReduceSum_module(input logic clk, enable, input logic [7:0] number, output logic [11:0]
sum, output logic [3:0] readAddress );

    logic [4:0] count = 5'b0;

    localparam constant = 5'b10000;

    logic [11:0] Sum = 12'b0;

    typedef enum logic [1:0] {S0, S1, S2, S3} statetype;

    statetype [1:0] state, nextState;


    // register

    always_ff @(posedge clk)

    begin

```

```

        state <= nextState;
end

// state transition
always_ff @ (posedge clk)
case(state)
    S0:
        begin
            if (enable)
                nextState <= S1;
            else
                nextState <= S0;
        end

    S1:
        begin
            count <= 4'b0;
            Sum <= 12'b0;
            nextState <= S2;
        end

    S2:
        begin
            if (count != constant) begin
                Sum = Sum + number;
                count = count + 1;
                nextState <= S2;
            end
        end
end

```

```

        end

    else

        nextState <= S3;

    end

S3:

    begin

        //Sum = Sum + number;

        sum = Sum;

        nextState <= S0;

    end

    default:

        nextState <= S0;

    endcase

    assign readAddress = count;

endmodule

```

Testbench for ReduceSum module:

```

module reducesum_testbench();

    logic clk, enable;

    logic [7:0] value;

    logic [11:0] sum;

    logic [3:0] address;

    ReduceSum_module dut( clk, enable, value, sum, address );

    always

```



```

begin

    clk = 1; #20; clk = 0; #20;

end

initial begin

    enable = 0; #10; enable = 1; sum = 0; address = 0;

    value = 8'b00000001;

end

endmodule

```

e) Write the SystemVerilog Code for the top design which will also include the Seven Segment Display and debouncer modules:

```

`timescale 1ns / 1ps

module TopModule( input logic clk, input logic [3:0] buttons, input logic [7:0] number,

    input logic [3:0] address, output logic [11:0] reduceSumSum, output logic [6:0] seg, output logic dp,
    output logic [3:0] an);

    logic [3:0] addressCounter;

    logic [3:0] reduceSumAddress;

    logic prev, next, enter, sum;

    logic [7:0] readData1, readData2;

    debounce previousButton(clk, buttons[3], prev);

    debounce nextButton(clk, buttons[2], next);

    debounce enterButton(clk, buttons[1], enter);

```

```

debounce sumButton(clk, buttons[0], sum);

always_ff @(posedge clk)
begin
    if ( prev) begin
        if ( addressCounter == 4'b0000) begin
            addressCounter <= 4'b1111;
        end
    else
        addressCounter <= addressCounter - 1;
    end

    else if ( next) begin
        if ( addressCounter == 4'b1111)
            addressCounter <= 4'b0000;
        else
            addressCounter <= addressCounter + 1;
        end
    end
end

memory_module mem( clk, enter, address, number, addressCounter, reduceSumAddress,
readData1, readData2);

SevSeg_4digit display( clk, addressCounter, 0, readData1[7:4], readData1[3:0], seg, dp, an);

ReduceSum_module reduceSum(clk, sum, readData2, reduceSumSum, reduceSumAddress);

endmodule

```