

CS223: Digital Design

Section 01


Lab 2

Efe Beydoğan

21901548

17.10.2020

 (b) Circuit schematic for a 2-bit adder made from two full adders:



(c) Behavioral SystemVerilog module for the full adder:

```
module behavioral_full_adder( input logic a, b, Cin, output logic sum, Cout);  
  
    assign sum = (a ^ b) ^ Cin;  
  
    assign Cout = ( ( a ^ b) & Cin) | ( a & b);  
  
endmodule
```

(d) Structural SystemVerilog module for the full adder and a testbench for it:

Structural SystemVerilog module for the full adder:

```
module structural_full_adder( input logic a, b, Cin, output logic sum, Cout);  
  
    logic n1, n2, n3; // internal nodes  
  
    xor( n1, a, b);  
  
    xor( sum, n1, Cin);  
  
    and( n2, n1, Cin);  
  
    and( n3, a, b);  
  
    or( Cout, n2, n3);  
  
endmodule
```

Testbench for the structural full adder:

```
module fulladder_testbench();

    logic a, b, Cin;

    logic sum, Cout;

    structural_full_adder dut( a, b, Cin, sum, Cout);

    initial begin

        a = 0; b = 0; Cin = 0; #10;

        if ( sum != 0 || Cout != 0) $display("000 failed");

        Cin = 1; #10;

        if ( sum != 1 || Cout != 0) $display("001 failed");

        b = 1; Cin = 0; #10;

        if ( sum != 1 || Cout != 0) $display("010 failed");

        Cin = 1; #10;

        if ( sum != 0 || Cout != 1) $display("011 failed");

        a = 1; b = 0; Cin = 0; #10;

        if ( sum != 1 || Cout != 0) $display("100 failed");

        Cin = 1; #10;

        if ( sum != 0 || Cout != 1) $display("101 failed");

        b = 1; Cin = 0; #10;

        if ( sum != 0 || Cout != 1) $display("110 failed");

        Cin = 1; #10;

        if ( sum != 1 || Cout != 1) $display("111 failed");

        end

    endmodule
```

(e) Structural SystemVerilog module for the full subtractor and a testbench for it:

Structural SystemVerilog module for the full subtractor:

```
module structural_full_subtractor( input logic a, b, Bin, output logic d, Bout);  
  
    logic n1, n2, n3; // internal nodes  
  
    xor( n1, a, b);  
  
    xor( d, Bin, n1);  
  
    and( n2, ~a, b);  
  
    and( n3, ~n1, Bin);  
  
    or( Bout, n3, n2);  
  
endmodule
```

Testbench for the structural full subtractor:

```
module fullsubtractor_testbench();  
  
    logic a, b, Bin;  
  
    logic d, Bout;  
  
  
    structural_full_subtractor dut( a, b, Bin, d, Bout);  
  
  
    initial begin  
  
        a = 0; b = 0; Bin = 0; #10;  
  
        if ( d != 0 || Bout != 0) $display("000 failed");  
  
        Bin = 1; #10;  
  
        if ( d != 1 || Bout != 1) $display("001 failed");  
  
        b = 1; Bin = 0; #10;  
  
        if ( d != 1 || Bout != 1) $display("010 failed");  
  
        Bin = 1; #10;  
  
        if ( d != 0 || Bout != 1) $display("011 failed");  
  
        a = 1; b = 0; Bin = 0; #10;
```

```

    if ( d != 1 || Bout != 0) $display("100 failed");

    Bin = 1; #10;

    if ( d != 0 || Bout != 0) $display("101 failed");

    b = 1; Bin = 0; #10;

    if ( d != 0 || Bout != 0) $display("110 failed");

    Bin = 1; #10;

    if ( d != 1 || Bout != 1) $display("111 failed");

    end

endmodule

```

(f) Structural SystemVerilog module for the 2-bit adder and a testbench for it:

Structural SystemVerilog module for the 2-bit adder:

```

module two_bit_adder( input logic a0, b0, Cin0, a1, b1, output logic Cout1, sum1, sum0);

    logic Cout0; // internal node

    behavioral_full_adder adder0( a0, b0, Cin0, sum0, Cout0);

    behavioral_full_adder adder1( a1, b1, Cout0, sum1, Cout1);

endmodule

```

Testbench for the structural 2-bit adder:

```

module twobitadder_testbench();

    logic a0, b0, Cin0, a1, b1;

    logic sum0, sum1, Cout1;

    two_bit_adder dut( a0, b0, Cin0, a1, b1, Cout1, sum1, sum0);

    initial begin

        a0 = 0; b0 = 0; Cin0 = 0; a1 = 0; b1 = 0; #10;
    end
endmodule

```

```
if ( sum0 != 0 || sum1 != 0 || Cout1 !=0) $display("00000 failed");

b0 = 1; #10;

if ( sum0 != 1 || sum1 != 0 || Cout1 !=0) $display("01000 failed");

b0 = 0; b1 = 1; #10;

if ( sum0 != 0 || sum1 != 1 || Cout1 !=0) $display("00001 failed");

b0 = 1; #10;

if ( sum0 != 1 || sum1 != 1 || Cout1 !=0) $display("01001 failed");

a0 = 1; b0 = 0; b1 = 0; #10;

if ( sum0 != 1 || sum1 != 0 || Cout1 !=0) $display("10000 failed");

b0 = 1; #10;

if ( sum0 != 0 || sum1 != 1 || Cout1 !=0) $display("11000 failed");

b0 = 0; b1 = 1; #10;

if ( sum0 != 1 || sum1 != 1 || Cout1 !=0) $display("10001 failed");

b0 = 1; #10;

if ( sum0 != 0 || sum1 != 0 || Cout1 !=1) $display("11001 failed");

a0 = 0; a1 = 1; b0 = 0; b1 = 0; #10;

if ( sum0 != 0 || sum1 != 1 || Cout1 !=0) $display("00010 failed");

b0 = 1; #10;

if ( sum0 != 1 || sum1 != 1 || Cout1 !=0) $display("01010 failed");

b0 = 0; b1 = 1; #10;

if ( sum0 != 0 || sum1 != 0 || Cout1 !=1) $display("00011 failed");

b0 = 1; #10;

if ( sum0 != 1 || sum1 != 0 || Cout1 !=1) $display("01011 failed");

a0 = 1; b0 = 0; b1 = 0; #10;

if ( sum0 != 1 || sum1 != 1 || Cout1 !=0) $display("10010 failed");

b0 = 1; #10;

if ( sum0 != 0 || sum1 != 0 || Cout1 !=1) $display("11010 failed");
```

```
b0 = 0; b1 = 1; #10;

if ( sum0 != 1 || sum1 != 0 || Cout1 !=1) $display("10011 failed");

b0 = 1; #10;

if ( sum0 != 0 || sum1 != 1 || Cout1 !=1) $display("11011 failed");

end

endmodule
```